

--	--	--	--	--	--	--	--

***B.Tech. Degree III Semester Supplementary Examination
November 2020***

**CS 15-1302 LOGIC DESIGN
(2015 Scheme)**


Time: 3 Hours

Maximum Marks: 60

**PART A
(Answer ALL questions)**

(10 × 2 = 20)

 - I. (a) Convert 2705_8 to its decimal and hexadecimal equivalent.
 (b) Simplify the following Boolean expression to minimum number literals:
 (i) $ABC + A'B + ABC'$
 (ii) $x'yz + xz$
 (c) Draw the NAND logic diagram of boolean function, $F = AB + BC + D$.
 (d) Draw the realization of half subtractor using gates.
 (e) What is a priority encoder?
 (f) Explain toggle flip-flop.
 (g) Draw the realization of twisted ring counter using D flipflop.
 (h) Differentiate between PROM and PAL.
 (i) Write the procedure for obtaining stable state of asynchronous sequential circuit.
 (j) What is propagation delay of a gate? Define setup time and hold time.



PART B

(4 × 10 = 40)

- II. (a) Using 10's complement, subtract 3250-72532. (2)
 (b) Write the rules of BCD addition and perform the BCD addition of (4)
 (i) $(8)_{10} + (9)_{10}$
 (ii) $(3)_{10} + (7)_{10}$
 (c) What are codes? Explain Weighted code and Unweighted codes with two examples. (4)

OR

- III. (a) Simplify the following Boolean functions using K-map (5)
 (i) $F(w,x,y,z) = \Sigma(0,1,2,4,5,6,8,9,12,13,14)$
 (ii) $F = ABCD + ACD + AD$
 (b) Minimize the following switching function using the Quine McCluskey method (5)
 $F(A,B,C,D) = \Sigma m(1,2,3,5,6,7,8,9,12,13,15)$.

- IV. (a) Explain the working of a 4-bit BCD adder with block diagram (7)
 (b) Write the procedure involved in design of combinational circuit. (3)


OR

- V. (a) Explain the working of a 4-bit magnitude comparator. (5)
 (b) Implement the following function with a multiplexer (5)
 $f(A,B,C,D) = \Sigma (0,1,3,4,11,12,13,14,15)$.

(P.T.O.)

BTS-III(S)-11.20-0662

 - VI. (a) Explain the working of SR latch with NAND gate with the help of logic diagram and function table. Which state is forbidden state? (6)
- (b) Draw the state table and state diagram for the circuit diagram. (4)



OR

- VII. Design a counter that has repeated sequence of six states 0,1,2,4,5,6 using JK flip-flop. (10)
- VIII. (a) Design a combinational circuit using a ROM. The circuit accepts three bit numbers and outputs a binary number equal to the square of the input number. (6)
- (b) Explain the working of PLA. (4)

OR

- IX. Explain the working of RTL and DTL circuit. Explain how fan-out of DTL gate can be increased? (10)
